

Intro to Verilog

□ TABLE 2-2

Verilog Primitives for Combinational Logic Gates

Gate primitive	Example instance
and	<code>and (F, X, Y);</code>
or	<code>or (F, X, Y);</code>
not	<code>not (F, Y);</code>
nand	<code>nand (F, X, Y);</code>
nor	<code>nor (F, X, Y);</code>
xor	<code>xor (F, X, Y);</code>
xnor	<code>xnor (F, X, Y);</code>

□ TABLE 2-4
Verilog Bitwise Logic Operators


Verilog operator symbol	Operator function	Example
~	Bitwise not	$F = \sim X;$
&	Bitwise and	$F = X \& Y;$
	Bitwise or	$F = X Y;$
^	Bitwise xor	$F = X ^ Y;$
~^, ^~	Bitwise xnor	$F = X \sim ^ Y;$

□ **TABLE 2-5**

Truth Table for the Function $L = D\bar{X} + A$

D	X	A	L
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

FIGURE 2-5 Logic Circuit Diagram for $L = DX + A$

 


Copyright ©2016 Pearson Education, All Rights Reserved

FIGURE 2-6 Verilog Model for the Logic Circuit of Figure 2-5

```
module fig2_5 (L, D, X, A);  
    input D, X, A;  
    output L;  
    wire X_n, t2;  
  
    not (X_n, X);  
    and (t2, D, X_n);  
    or (L, t2, A);  
endmodule
```

Copyright ©2016 Pearson Education, All Rights Reserved

FIGURE 2-27 Gate level schematic for a two-bit greater-than comparator circuit

 

Copyright ©2016 Pearson Education, All Rights Reserved

FIGURE 2-33 Structural Verilog Description of Two-Bit Greater-Than Circuit

```
// Two-bit greater-than circuit: Verilog structural model           // 1
// See Figure 2-27 for logic diagram                               // 2
module comparator_greater_than_structural(A, B, A_greater_than_B); // 3
    input [1:0] A, B;                                              // 4
    output A_greater_than_B;                                       // 5
    wire B0_n, B1_n, and0_out, and1_out, and2_out;               // 6
    not                                              // 7
        inv0(B0_n, B[0]), inv1(B1_n, B[1]);                       // 8
    and                                              // 9
        and0(and0_out, A[1], B1_n),                               // 10
        and1(and1_out, A[1], A[0], B0_n),                       // 11
        and2(and2_out, A[0], B1_n, B0_n);                       // 12
    or                                              // 13
        or0(A_greater_than_B, and0_out, and1_out, and2_out);    // 14
endmodule                                                    // 15
```

Copyright ©2016 Pearson Education, All Rights Reserved

FIGURE 2-34 Dataflow Verilog Description of Two-Bit Greater-Than Comparator

```
// Two-bit greater-than circuit: Dataflow model // 1
// See Figure 2-27 for logic diagram // 2
module comparator_greater_than_dataflow(A, B, A_greater_than_B); // 3
    input [1:0] A, B; // 4
    output A_greater_than_B; // 5
    wire B1_n, B0_n, and0_out, and1_out, and2_out; // 6
    assign B1_n = ~B[1]; // 7
    assign B0_n = ~B[0]; // 8
    assign and0_out = A[1] & B1_n; // 9
    assign and1_out = A[1] & A[0] & B0_n; // 10
    assign and2_out = A[0] & B1_n & B0_n; // 11
    assign A_greater_than_B = and0_out | and1_out | and2_out; // 12
endmodule // 13
```

Copyright ©2016 Pearson Education, All Rights Reserved

FIGURE 2-35 Conditional Dataflow Verilog Description of Two-Bit Greater-Than Circuit

```
// Two-bit greater-than circuit: Conditional model // 1
// See Figure 2-27 for logic diagram // 2
module comparator_greater_than_conditional2(A, B, A_greater_than_B); // 3
    input [1:0] A, B; // 4
    output A_greater_than_B; // 5
    assign A_greater_than_B = (A > B)? 1'b1 : // 6
        1'b0; // 7
endmodule // 8
```

Copyright ©2016 Pearson Education, All Rights Reserved

FIGURE 2-37 Behavioral Verilog Description of Two-Bit Greater-Than Circuit

```
// Two-bit greater-than circuit: Behavioral model // 1
// See Figure 2-27 for logic diagram // 2
module comparator_greater_than_behavioral(A, B, A_greater_than_B); // 3
    input [1:0] A, B; // 4
    output A_greater_than_B; // 5
    assign A_greater_than_B = A > B; // 6
endmodule // 7
```

Copyright ©2016 Pearson Education, All Rights Reserved

THE END